

## 2022 Digital IC Design Homework 2

NAME	陳柏均				
Student ID	P76101584				
Functional Simulation Result					
Stage 1	Pass	Stage 2	Pass	Stage 3	Pass
Stage 1					
<pre># --stage1 simulation-- # # Setting1: PASS # # Setting2: PASS # # Setting3: PASS # # Setting4: PASS # # Setting5: PASS # # Setting6: PASS # # Setting7: PASS # # Setting8: PASS # # Setting9: PASS # # Setting10: PASS #</pre>					
Stage 2					
<pre># --stage2 simulation-- # # Setting11: PASS # # Setting12: PASS # # Setting13: PASS # # Setting14: PASS # # Setting15: PASS # # Setting16: PASS # # Setting17: PASS # # Setting18: PASS # # Setting19: PASS # # Setting20: PASS # #</pre>					
Stage 3					

```

# --stage3 simulation--
#
# Setting21: PASS
#
# Setting22: PASS
#
# Setting23: PASS
#
# Setting24: PASS
#
# Setting25: PASS
#
# Setting26: PASS
#
# Setting27: PASS
#
# Setting28: PASS
#
# Setting29: PASS
#
# Setting30: PASS
#

```

### Description of your design

主要分為: controller 模組和 data path 模組，

其中 data path 模組又分為 counter 模組、compare 模組。

● Controller: 以兩個 combinational circuit 和一個 Sequential circuit 組成  
燈號順序為: 綠、黃、紅、綠....

Sequential circuit: state register

If Set = 1 or reset = 1: current state = green light

If Jump = 1: current state = red light

If Stop = 1: current state = current state

Else current state = next state

1<sup>st</sup> combinational circuit: next state logic

根據 current state:

If recount = 1 => next state 為下一個燈號順序，否則保持原燈號。

2<sup>nd</sup> combinational circuit: output logic

根據 current state 決定 control signal

● Counter: 一個 Sequential circuit 組成

If (rst | Jump | Set | Recount\_counter) => count out = 1

If Stop => count out = count out

Else count out = count out + 1

● Compare: 以一個 combinational circuit 和一個 Sequential circuit 組成

Sequential circuit: 儲存各燈號秒數

If Set = 1 => 將 Rin, Yin, Gin 存入 register

Sequential circuit: 比較 counter 是否等於對應燈號秒數，如果等於，將  
recount 設為 1，否則 recount = 0